# KGP RISC Instruction Format and Encoding

**Group 32** 

Anirban Haldar (20CS10008) Saikat Moi (20CS10050)

#### **Instruction Formats:**

Instruction formats are of the following 3 formats:

- 1. R (register) Format
- 2. I (Immediate) Format
- 3. J (Jump) Format

#### **R-Format:**

Field Size	6	5	5	5	6	5	Instructions
R-format	ор	rs	rt	shamt	func	dc	Add, cmp, and, xor, all-shift instructions

At present, all R-format instructions are kept under the same op-code:

#### Op-code - **000000**

Instruction	Function Code
Add	1
Comp	2
AND	3
XOR	4
shll	1100
shrl	1110
shra	1111
shrav	1011
shrlv	1010
shllv	1000
dff	

## **I-Format:**

Field-size	6	5	5	16	Instructions
I-format	ор	rs	rt/ dc	address/ immediate	addi, compi, lw, sw

The table given below gives the op-code for all the above instructions:

Instruction	op-code
addi	001000
compi	001010
lw	010000
sw	010010

## J-Format:

Field Size	6	26	Instructions
J-Format	ор	Target address	b, br, bl, bcy, bncy

The table given below gives the op-code for all the above instructions:

Instruction	op-code	fmt
b	100000	op   rs   xxxxxxxx
b	101000	op   label
bny	101001	op   label
bncy	101010	op   label
bl	101011	op   label

bltz	110000	op   rs   xx   label
bz	110001	op   rs   xx   label
bnz	110010	op   rs   xx   label

## **Register Convention:**

The architectural design is to be used in a similar fashion as per the MIPS convention for regular use as mentioned:

Symbolic Name	Number	Use
zero	0	Constant 0
at	1	Reserved for assembler
v0 - v1	2-3	Result registers
a0 - a3	4-7	Argument registers
t0 - t9	8 - 15, 24 - 25	Temporary registers
s0 - s7	16 - 23	Saved registers
k0 - k1	26 - 27	Kernel registers
gp	28	Global Data Pointer
sp	29	Stack Pointer
fp	30	Frame Pointer
ra	31	Return Address

## **ALU Design:**

#### **ALU Flags:**

- 1. Zero
- 2. Sign (0 if positive, 1 for negative)
- 3. Carry

ALU-operation funcode[3]		funcode[2]	funcode[1]	funcode[0]	
forward	vard 0 0		0	0	
add 0		compl/ not-compl	0	1	
and	0	0	1	0	
xor	0	0	1	1	
shift 1		shamt/ reg	right/ left	log/ arithm	

# Truth table for ALU control signals:

operation	opcode	funcode	alucode[3]	alucode[2]	alucode[1]	alucode[0]
add	000000	000001	0	0	0	1
comp	000000	000101	0	1	0	1
addi	001000	-	0	0	0	1
compi	001001	-	0	1	0	1
and	000000	000010	0	0	1	0
xor	000000	000011	0	0	1	1
shll	000000	001100	1	1	0	0
shrl	000000	001110	1	1	1	0

shllv	000000	001000	1	0	0	0
shrlv	000000	001010	1	0	1	0
shra	000000	001111	1	1	1	1
shrav	000000	001011	1	0	1	1
lw	010000	-	0	0	0	1
sw	011000	-	0	0	0	1
b	101000	-	0	0	0	0
br	100000	-	0	0	0	0
bltz	110000	-	0	0	0	0
bz	110001	-	0	0	0	0
bnz	110010	-	0	0	0	0
bl	101011	-	0	0	0	0
bcy	101001	-	0	0	0	0
bncy	101010	-	0	0	0	0

## **ISA Datapath and Control Signals:**

There are 3 main ways in which instruction memory can be referenced to in the instruction set:

- 1. Direct PC addressing
- 2. PC-relative addressing
- 3. (Pseudo) Direct Jump Addressing

#### **Direct Addressing:**

This type of addressing takes place for 'br' instruction where the argument register has the exact address to jump to.

#### PC Relative Addressing:

This type of addressing takes in any 16-bit Label instruction like bz, bnz, blitz where the absolute address is calculated using the following formula:

Address = (PC + 4) + SignExtended (Label)

#### Pseudo Direct Addressing:

This type of addressing takes in any 26-bit label instruction like b, bl, bcy, bncy where the absolute address is calculated using the following formula:

 $Address = \{(PC + 4)[31:28], \{Label, 2b'00\}\}$ 

## **Control Signals:**

- 1. Rewrite: to decide whether to write into the register file or not
- 2. RegDst[1:0]: for the destination register for the write-register (can be \$ra, rs, rt)
- 3. ALUSrc: for the Source for the 2nd input to the ALU (can be rt, sgn-extend(imm))
- 4. MemRead: to decide whether to read from Data Memory or not
- 5. MemWrite: to decide whether to write into the Data Memory or not
- Mem2Reg[1:0]: for write-data for the register files (can be one of: PC+4, mem[], result\_ALU)
- 7. LblSel: for select type of addressing for PC-Relative and PseudoDirect
- 8. JumpAdd: to decide whether the jump address comes from a source reg (rs) or from a label

# **Truth Table for control signals**

Ор	Opcode	RegDst	RegWrite	ALUSrc	MemRead	MemWrite	Mem2Reg	LbISel	JumpSel
add	000000	00	1	0	0	0	00	х	х
comp	000000	00	1	0	0	0	00	х	х
addi	001000	00	1	1	0	0	00	х	х
compi	001001	00	1	1	0	0	00	х	x
and	000000	00	1	0	0	0	00	х	x
xor	000000	00	1	0	0	0	00	х	x
shll	000000	00	1	0	0	0	00	х	x
shrl	000000	00	1	0	0	0	00	х	х
shllv	000000	00	1	0	0	0	00	х	х
shrlv	000000	00	1	0	0	0	00	х	х
shra	000000	00	1	0	0	0	00	х	х
shrav	000000	00	1	0	0	0	00	х	х
lw	010000	01	1	1	1	0	01	х	х
sw	011000	х	0	1	0	1	х	х	х
b	101000	х	0	х	0	0	х	0	0
br	100000	х	0	х	0	0	х	х	1
bltz	110000	х	0	х	0	0	х	1	0
bz	110001	х	0	х	0	0	х	1	0
bnz	110010	х	0	х	0	0	х	1	0
bl	101011	10	1	х	0	0	10	0	0
bcy	101001	х	0	х	0	0	х	0	0
bncy	101010	х	0	х	0	0	х	0	0



